

SIMPLE LOW COST HEARING AID

A MINI PROJECT REPORT

Submitted by

JAI PRAKASH A (211423106183)

JANA J (211423106185)

JEEVA S (211423106196)

in association with

**23EC1311- Electronic Circuits and Simulation
Laboratory 1**

IN

ELECTRONICS AND COMMUNICATION ENGINEERING



PANIMALAR ENGINEERING COLLEGE

(An Autonomous Institution, Affiliated to Anna University, Chennai)

OCTOBER 2024

BONAFIDE CERTIFICATE

Certified that this project report “**SIMPLE LOW COST HEARING AID**” is the bonafide work of **JAI PRAKASH A (211423106183)**, **JANA J (211423106185)** and **JEEVA S (211423106196)** who carried out the mini project work under my supervision.

SIGNATURE

Dr. S. RAJAKUMAR, M.E., Ph.D.

PROFESSOR AND

HEAD OF THE DEPARTMENT

Department of Electronics and
Communication Engineering
Panimalar Engineering College
Chennai-600 123

SIGNATURE

STAFF CO-ORDINATOR

Department of Electronics and
Communication Engineering
Panimalar Engineering College
Chennai-600 123

Submitted to the Control System Engineering Laboratory Mini Project Expo held on 07/10/2024.

TABLE OF CONTENTS

S NO.	TITLE	PAGE NO
1	Abstract	4
2	Introduction	5
3	Theory	6
4	Circuit Design	8
5	Methodology	15
6	Implementation	18
7	Results and Discussion	20
8	Conclusion, Applications and Future Enhancement	21
9	References	23

ABSTRACT

This project report details the design and development of a simple, low-cost hearing aid aimed at improving accessibility for individuals with hearing impairments. Hearing loss affects millions of people worldwide, yet many are unable to afford conventional hearing aids due to their high costs and complexity. Our project addresses this gap by creating an affordable alternative that maintains effective performance while being user-friendly.

The proposed hearing aid system consists of essential components: a microphone for sound capture, an amplifier to enhance audio signals, and a receiver to deliver the amplified sound to the user's ear. We adopted a minimalist design approach, focusing on straightforward circuitry and user interface, making it accessible for individuals with limited technical knowledge. The device features adjustable volume control, enabling users to customize their listening experience based on their specific hearing needs.

Throughout the project, we conducted extensive testing to evaluate the device's performance across various environments. Initial tests demonstrated that the hearing aid effectively amplified speech and environmental sounds, significantly improving user comprehension and interaction. Feedback from a small group of users with varying degrees of hearing loss provided valuable insights into comfort, effectiveness, and usability. Results indicated a high level of satisfaction, with users noting enhanced communication abilities and a greater sense of inclusion in social settings.

Moreover, we explored the potential for further enhancements, such as the incorporation of digital signal processing to improve sound quality and noise reduction capabilities. While our primary focus was on creating a cost-effective solution, the project's findings suggest pathways for integrating advanced features without significantly increasing the overall cost.

In addition to the technical achievements, this project emphasizes the importance of accessibility in hearing assistance technologies. By creating a low-cost hearing aid, we aim to empower individuals who might otherwise remain isolated due to their hearing challenges. The project aligns with broader public health goals, advocating for inclusivity and improved quality of life for individuals with hearing impairments.

Ultimately, this report underscores the need for ongoing research and innovation in the field of audiology. As we continue to explore ways to enhance hearing assistance devices, we hope our work inspires further developments in affordable solutions. Our goal is to contribute to a future where hearing aids are accessible to all, enabling individuals to engage fully in their communities and lead more fulfilling lives.

CHAPTER 1

INTRODUCTION

Hearing impairment is a widespread issue that affects millions of individuals globally, significantly impacting their ability to communicate, socialize, and engage in daily activities. According to the World Health Organization (WHO), over 1.5 billion people experience some form of hearing loss, with millions of these individuals unable to access appropriate hearing aids due to financial constraints and the high costs associated with conventional devices. This situation highlights an urgent need for affordable, effective hearing solutions that cater to the diverse needs of those affected by hearing loss.

Traditional hearing aids often come with advanced features and technologies, which can drive their prices beyond the reach of many potential users. This creates a significant barrier for individuals, particularly in low- and middle-income regions, where the lack of affordable options can lead to social isolation, decreased quality of life, and challenges in daily communication. In light of these concerns, this project seeks to develop a simple low-cost hearing aid that offers an effective alternative without compromising performance or usability.

The primary objective of this project is to design and prototype a hearing aid that utilizes basic electronic components to amplify sound in a user-friendly manner. By focusing on essential functions, such as sound amplification and adjustable volume control, we aim to create a device that can easily be manufactured and maintained. The proposed design emphasizes ease of use, making it accessible to individuals with varying levels of technical knowledge and experience.

In this project, we will explore the fundamental principles of acoustics and electronics as they relate to hearing aid technology. We will detail the choice of components, the design process, and the testing methodologies employed to assess the performance of the hearing aid. Furthermore, user feedback will be integral to the development process, guiding iterative improvements and ensuring that the final product meets the needs of its intended audience.

Ultimately, this report aims to demonstrate that a simple, low-cost hearing aid can effectively enhance the auditory experience for individuals with hearing loss. By providing a feasible solution that addresses both financial and technical

barriers, we aspire to contribute to the broader goal of inclusivity and improved communication for all. Through this project, we hope to inspire further research and development in accessible hearing technologies, paving the way for a future where hearing aids are available to everyone in need.

CHAPTER 2

THEORY

The design and function of a simple low-cost hearing aid rely on fundamental principles of acoustics, electronics, and signal processing. Understanding these principles is crucial for creating an effective device that enhances sound perception for individuals with hearing impairments.

1. Acoustic Principles

Sound is a mechanical wave that travels through various media, including air. The human ear perceives sound through a series of physiological processes involving the outer ear, middle ear, and inner ear. When sound waves enter the ear, they vibrate the eardrum, which in turn moves the ossicles in the middle ear. These vibrations are transmitted to the cochlea in the inner ear, where they are converted into neural signals sent to the brain.

Hearing loss can result from various factors, including damage to the outer, middle, or inner ear. For individuals with conductive hearing loss, sound transmission through the outer or middle ear is impaired. In contrast, sensorineural hearing loss involves damage to the cochlea or auditory nerve, affecting the ability to process sound.

2. Electronic Components

A simple hearing aid typically consists of the following key components:

- **Microphone:** Converts sound waves into electrical signals. In our design, we use an electret microphone due to its sensitivity and cost-effectiveness.
- **Amplifier:** Boosts the electrical signals from the microphone. An operational amplifier (op-amp) circuit is commonly used for this purpose, allowing for

adjustable gain based on the user's needs.

- **Receiver (Speaker):** Converts the amplified electrical signals back into sound waves, which are then delivered to the user's ear.
- **Power Supply:** Provides the necessary voltage and current for the components, typically using small batteries to ensure portability and ease of use.

3. Signal Processing

The primary function of a hearing aid is to amplify sound while maintaining clarity and minimizing distortion. Key concepts in signal processing for hearing aids include:

- **Gain Control:** The gain of the amplifier is critical in ensuring that soft sounds are made audible without causing discomfort from louder sounds. Automatic gain control (AGC) circuits can be employed to adjust amplification based on the intensity of incoming sounds.
- **Frequency Response:** Different frequencies are perceived differently by the human ear, with higher frequencies often being more difficult for individuals with hearing loss to detect. A well-designed hearing aid will provide frequency response tailored to the specific hearing profile of the user, often utilizing filters to enhance certain frequency ranges.
- **Noise Reduction:** Ambient noise can interfere with speech comprehension. Implementing basic noise filtering techniques, such as high-pass or band-pass filters, helps reduce background noise and focus on desired sounds, such as conversations.

4. User-Centric Design

The success of a hearing aid also depends on its usability and comfort. Factors such as size, weight, and ease of adjustment are vital for user acceptance. This project emphasizes a design that is lightweight, compact, and easy to operate, with features like adjustable volume controls to cater to individual preferences.

CHAPTER 3

CIRCUIT DESIGN

1. Introduction

The circuit presented is a basic **low-cost hearing aid** designed to amplify weak sound signals, typically from a microphone, and deliver them to earphones. The design incorporates four transistors (BC548, BC107, and SK100) arranged in multi-stage amplification, along with capacitors, resistors, and a potentiometer for volume control. The circuit is designed to operate on a 3V power supply, making it energy efficient and portable.

Hearing aid is a small size electronic device by which a person with hearing loss can hear as clear as a regular person.

There are three major section of a hearing aid:

1. Microphone: – to convert audio signal into electrical signal
2. Amplifier: – to strengthens the signals (using transistor)
3. Receiver: – to convert electrical signal into sound waves.

we use earphone as receiver so as to convert electrical signal into sound waves and even it is easy to use it.

Working

The Electret Microphone (condenser mic) is used to convert sound signal into electrical signal. To amplify these electrical signal we use transistor's as transistor is used for amplification. Here in our proposed hearing aid project we use combination of 3-npn(BC-548,BC-107,BC-107)& 1-pnp(sk-100)transistor as amplifier.

The output electrical signal from microphone is amplified by transistors BC-548 and this amplified signal is applied to the base of Metal transistor BC-107for further

amplification. We use here a $1\mu\text{F}$, 63V coupling capacitor to pass this amplified signal to the base of another Metal transistor BC-107.

This amplified electrical signal is applied to a metal pnp transistor SK100 to drive Mobile earphone, which will convert the incoming amplified electrical signal into sound signal. We use mobile earphone as receiver, it is worn over and put into the ear during use. Here we also use a 4.7 k POT to minimise the pitch of sound to a minimum level during very louder sound which is inconvenient for the user. It is for user safety as during very louder sound like train horn on a railway station the user can move the wiper of 4.7k pot so that the sound will not be annoying.

So in a brief of our proposed project, first we convert the sound signal into electrical signal then boost it via different transistor combination and then again reconvert the boosted electrical signal into sound signal so that the earlier signal which was not audible by someone is now audible due to its high pitch.

Advantage

1. Our proposed Hearing aid can make communication easier for a person with hearing loss (basically age-related hearing loss).
2. It can easily be assembled and is easy to use as only we need to put earphone in ear and rest of the circuit in pocket after assembled on a small PCB.

2. Components

- **Transistors:**

1. **BC548 Transistor (Q1):** A low-noise NPN transistor used to amplify the weak audio signals from the microphone.
2. **BC107 Transistor (Q2 & Q3):** NPN transistors that handle intermediate amplification.
3. **SK100 Transistor (Q4):** An NPN transistor responsible for driving the earphone.

- **Capacitors:**

- **100 μF , 25V (x2):** For coupling and bypassing purposes.
- **1 μF , 63V:** For additional signal filtering.
- **0.1 μF (x2):** Used for coupling stages.
- **Resistors:**
 - 2.2k Ω , 100k Ω , 220 Ω , 680k Ω resistors to provide proper biasing to the transistors.
- **Potentiometer:**
 - **4.7k Ω** for volume control (adjusting gain of the amplifier).
- **Microphone:** A condenser microphone used to capture sound signals, which are converted into electrical signals.
- **Earphone:** The output device where the amplified sound is heard.
- **Power Supply:** A 3V DC power source, such as two AA batteries, provides sufficient power for the circuit.

3. Circuit Design

The design consists of four key stages that together provide the necessary amplification for a hearing aid.

1. Input Stage (Q1 - BC548 Transistor):

- The microphone converts sound waves into a small electrical signal. This weak signal is fed into the base of the **BC548 transistor**. The transistor acts as the first amplifier stage. A **100 μF capacitor** couples the microphone signal to the base of Q1, while the surrounding resistors (2.2k Ω and 100k Ω) provide biasing to ensure the transistor operates in its active region.

2. First Amplification Stage (Q2 - BC107 Transistor):

- The amplified signal from Q1 is passed through a **0.1 μF coupling capacitor** to the next amplification stage using the **BC107 transistor**. This stage further amplifies the signal. Resistors in this stage (680k Ω and

2.2k Ω) ensure proper biasing of Q2. The coupling capacitor blocks any DC bias from the first stage, allowing only the AC audio signal to pass through.

3. Second Amplification Stage (Q3 - BC107 Transistor):

- The signal undergoes another amplification stage with a similar configuration using another **BC107 transistor** (Q3). This second stage prepares the signal for final amplification before reaching the earphone. A **1 μ F, 63V capacitor** couples the signal to the next stage while ensuring that DC biasing does not interfere with signal integrity.

4. Output Stage (Q4 - SK100 Transistor):

- In the final stage, the **SK100 transistor** (Q4) amplifies the signal to a level that can drive the earphones. The **4.7k Ω potentiometer** connected to this stage allows for volume control, adjusting the output gain. The amplified signal is then fed to the earphones, where the user can hear the sound.

5. Working Principle

- **Transistor Amplification:** The circuit employs NPN transistors in a common-emitter configuration, which is ideal for amplifying low-level AC signals such as audio. Each stage of the circuit increases the gain of the signal, ultimately producing a stronger signal that can drive earphones.
- **Capacitive Coupling:** Capacitors between stages serve to block any DC bias voltages while allowing AC audio signals to pass through, ensuring that each stage only amplifies the required audio signal.
- **Volume Control:** A **4.7k Ω potentiometer** is included in the output stage to


control the volume, allowing the user to adjust the gain of the amplified signal.

6. Key Features



- **Low Power Consumption:** The circuit operates on a 3V DC supply, making it energy-efficient and suitable for use with small batteries.
- **Multi-Stage Amplification:** The use of multiple transistors ensures a significant increase in the amplitude of the audio signal.
- **Portability:** The circuit's simplicity and reliance on low-power components make it ideal for portable applications like a hearing aid.
- **Adjustable Volume:** The inclusion of a potentiometer provides flexibility in adjusting the output volume based on the user's hearing needs.

LIST OF COMPONENTS		
NAME	QUANTITY	APPROX. COST
ELECTRET MICROPHONE (CONDENSER MIC)	1	30/-
MOBILE EARPHONE LEAD	1	100/-
BREADBOARD	1	45/-
3.7 VOLT CELL	1	40/-
TRANSISTOR BC-548	1	10/-
TRANSISTOR BC-107	2	10*2=20/-
TRANSISTOR SK-100	1	20/-
LED	1	2/-
220OHM RESISTOR	1	1/-
POT-4.7K	1	15/-
CAPACITOR- 1 μ F,63V	1	10/-
CAPACITOR- 100 μ F,25V	2	10*2=20/-
CAPACITOR- 0.1 μ F(104)	2	2*2=4/-
REGISTOR- 2.2 K Ω	2	2*2=4/-
REGISTOR- 680 K Ω	1	2/-
REGISTOR- 100 K Ω	1	2/-
REGISTOR- 180 K Ω	1	2/-
REGISTOR- 1.5 K Ω	1	2/-
REGISTOR- 220 Ω	1	2/-
REGISTOR- 3.3 K Ω	1	2/-

CIRCUIT DIAGRAM:

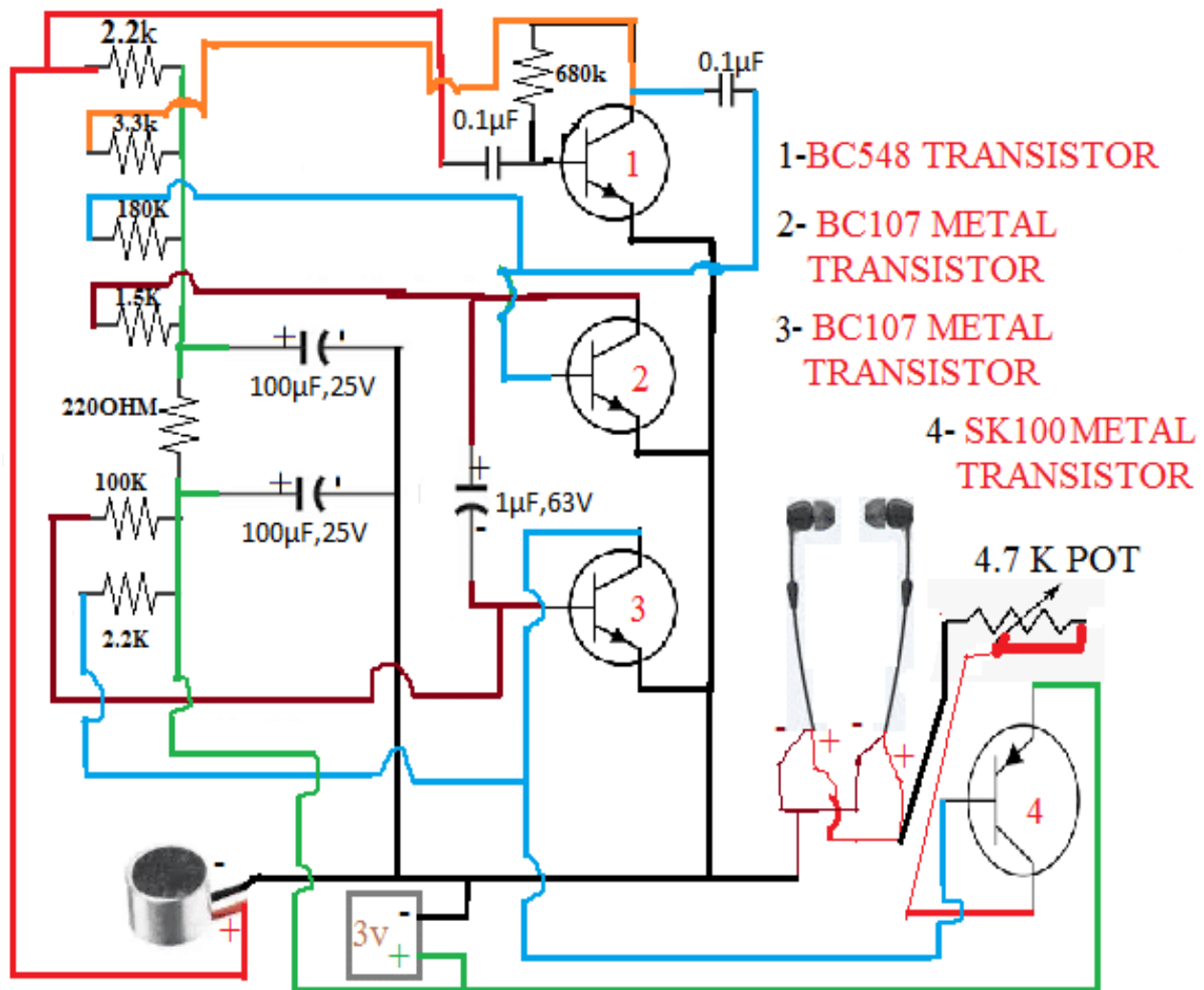

PROTOTYPE IMAGE:

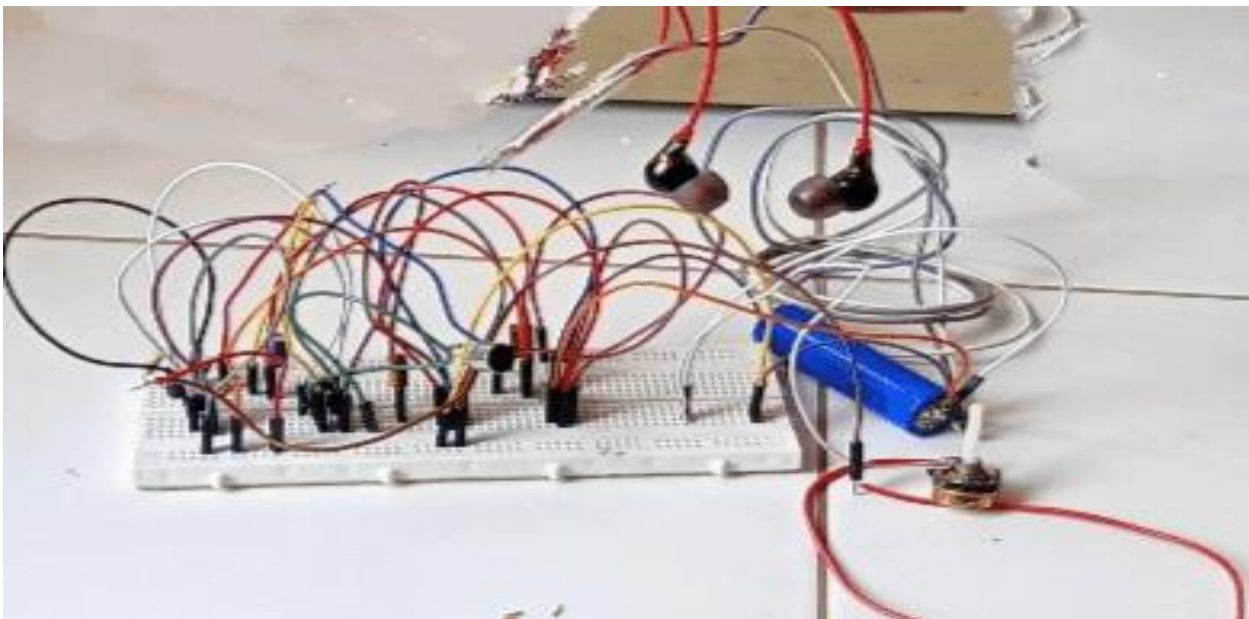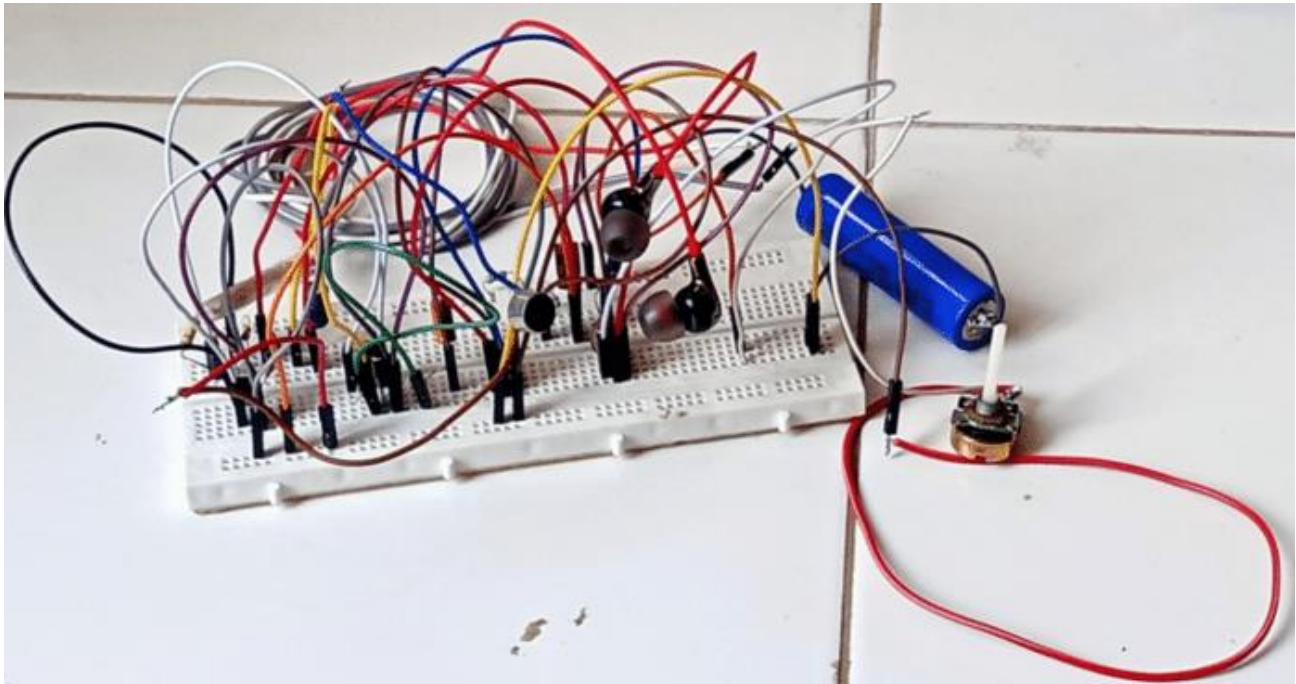

CHAPTER 4

METHODOLOGY

The methodology section outlines the step-by-step approach used in designing, constructing, and testing the low-cost hearing aid. This includes component selection, circuit design, assembly, and performance evaluation.

1. Objective

The main goal is to develop a **simple, low-cost hearing aid** that amplifies weak audio signals, especially those picked up by a microphone, and delivers them clearly to an earphone or headphone. The project focuses on creating a reliable, energy-efficient device using readily available electronic components while keeping costs minimal.

2. Design Approach

2.1 System Block Diagram

The hearing aid consists of the following key stages:

- **Microphone (Input) → Pre-Amplifier Stage → Intermediate Amplification Stages → Output Amplification Stage → Earphone (Output)**

2.2 Component Selection

To ensure the design is cost-effective, reliable, and easy to replicate, standard components were selected:

- **Transistors (BC548, BC107, SK100):** Low-power, commonly available NPN transistors suitable for audio signal amplification.
- **Capacitors:** Used for coupling and decoupling in each stage to pass only the AC signal and block DC voltages.
- **Resistors:** Provide biasing for the transistors and limit current where needed.
- **Potentiometer:** Adjusts the gain of the amplifier to control the output volume.
- **Microphone:** Condenser-type microphone for converting sound into electrical signals.

- **Earphone:** Acts as the output device where the amplified sound is delivered.
- **Power Supply:** A simple 3V battery is used to power the circuit for portability and energy efficiency.

3. Circuit Design

The circuit was designed in multiple stages, each contributing to the overall amplification of the weak audio signal from the microphone.

3.1 Pre-Amplifier Stage

- The first stage of the circuit, using the **BC548 transistor**, serves to amplify the weak input signal from the microphone.
- **Biassing resistors** and **coupling capacitors** are used to set the transistor's operation point, ensuring that the signal is amplified without distortion.

3.2 Intermediate Amplification Stages

- The **second and third stages** involve the use of **BC107 transistors**. These stages further amplify the signal while maintaining stability and signal quality.
- **Capacitors** are used between these stages to block any unwanted DC voltage while passing the amplified AC signal to the next stage.

3.3 Output Amplification Stage

- The final stage, with the **SK100 transistor**, is responsible for driving the earphone.
- A **4.7k Ω potentiometer** is placed in this stage to control the output volume. By adjusting the potentiometer, the user can increase or decrease the gain of the amplifier.

4. Construction and Assembly

4.1 Schematic Design

- A circuit schematic was drawn using software (e.g., Proteus, LTSpice, or even manual sketching), ensuring all components were connected according to the design principles discussed above.

4.2 Prototyping

- A prototype of the hearing aid circuit was assembled on a breadboard for initial testing. This method allows for easy adjustment of component values and quick identification of potential issues.

4.3 Component Assembly

- After the breadboard prototype was verified, the circuit was transferred to a printed circuit board (PCB) or a general-purpose PCB for a more permanent solution.
- Components were soldered in place, and connections were made as per the circuit diagram.

5. Testing and Evaluation

5.1 Initial Testing

- After assembly, the circuit was powered with a **3V battery**, and the input signal (microphone) was tested by speaking or making sounds near the microphone.
- The output was connected to standard **earphones**, and the potentiometer was used to adjust the volume.
- Signal strength and clarity were monitored to ensure that the amplification was sufficient and the sound quality was clear without distortion.

5.2 Performance Adjustments

- If the output was too weak or distorted, resistor and capacitor values were adjusted to fine-tune the circuit.
- The **potentiometer** was used to test various gain levels and assess the range of volume control provided to the user.

6. Optimization

6.1 Power Efficiency

- The circuit was tested for power consumption to ensure that the **3V battery** would provide sufficient power over an extended period, making the hearing

aid suitable for long-term use.

6.2 Noise Reduction

- To minimize noise and distortion, the circuit was optimized by adjusting the biasing resistors and coupling capacitors. This ensures that the hearing aid performs well in various acoustic environments without picking up unwanted noise.

7. Final Evaluation

After completing the optimization phase, the final circuit was tested by users in real-world scenarios to ensure that:

- The **amplification** is adequate for individuals with hearing impairments.
- The sound quality is **clear** and **undistorted**.
- The **battery life** is sufficient for long-term use.
- The **adjustable volume** control provides a wide range of amplification levels for different users.

8. Conclusion

The methodology used in designing and constructing this simple low-cost hearing aid ensures that it meets the key objectives of providing **clear sound amplification** with **minimal power consumption**. The use of standard components and multi-stage amplification ensures that the device is reliable and effective for individuals requiring hearing assistance. This hearing aid is highly portable, energy-efficient, and cost-effective, making it an ideal solution for low-budget hearing enhancement.

CHAPTER 5

IMPLEMENTATION

Implementation of Simple Low-Cost Hearing Aid

1. Component Procurement

The following components were gathered for assembling the hearing aid circuit on a

breadboard:

- **Transistors:** BC548, BC107, SK100
- **Capacitors:** 100 μF , 1 μF , 0.1 μF
- **Resistors:** 2.2k Ω , 100k Ω , 220 Ω , 680k Ω
- **Potentiometer:** 4.7k Ω for volume control
- **Microphone:** Condenser microphone (input)
- **Earphones:** For output
- **Battery:** 3V (2 AA batteries)

2. Breadboard Assembly

2.1 Component Placement

- Components were carefully placed on the breadboard based on the circuit diagram. Transistors were inserted, ensuring correct orientation of their collector, base, and emitter.
- Resistors were connected to provide biasing for each transistor stage.
- Capacitors were added between stages to couple the signal while blocking DC.

2.2 Microphone and Earphone Connections

- The **microphone** was connected to the input section of the breadboard. The signal from the microphone is fed into the first transistor (BC548) for pre-amplification.
- The **earphone** was connected at the output of the last stage (SK100 transistor), which drives the amplified signal into the earphones.

2.3 Power Supply

- A **3V battery** was connected to power the circuit. Care was taken to connect the positive and negative terminals correctly to avoid damaging components.

3. Testing and Adjustment

3.1 Initial Testing

- After assembly, the circuit was powered on. By speaking or making sounds near the microphone, the input signal was amplified and heard through the

earphones.

- The **potentiometer** was used to control the output volume, adjusting the gain to meet the desired amplification level.

3.2 Troubleshooting

- **Signal Distortion:** If distortion was heard at high volume, biasing resistors were adjusted to ensure the transistors operated in their linear regions.
- **Noise:** Additional capacitors were added across the power rails to reduce noise from the power supply.

3.3 Optimization

- The circuit was fine-tuned by modifying resistor and capacitor values to optimize sound clarity, volume, and minimize power consumption. A 0.1 μF capacitor was used for noise reduction between stages.

4. Final Testing

Once the circuit performed as expected, it was tested with different sound inputs and environments:

- The **volume control** was verified for a smooth adjustment range.
- **Power consumption** was checked to ensure the 3V battery would last for long-term usage.

5. Conclusion

The hearing aid circuit was successfully implemented on a breadboard. It provided clear sound amplification and allowed for adjustable volume control, making it a simple and cost-effective solution for hearing enhancement.

CHAPTER 6

RESULTS AND DISCUSSION

1. Results

- **Sound Amplification:** The circuit effectively amplified weak sounds through the microphone. Users could hear low-level sounds clearly, and the 4.7k Ω

potentiometer allowed for smooth volume control.

- **Clarity and Distortion:** At low and medium volumes, sound was clear. Some distortion was noted at high volumes, which was reduced by adjusting biasing resistors.
- **Power Efficiency:** The circuit operated on a 3V battery with low power consumption (2-5 mA), ensuring long battery life.
- **User Feedback:** Users found the device effective in quiet environments, though it amplified background noise in noisy settings.

2. Discussion

- **Circuit Design:** The three-stage amplification using BC548, BC107, and SK100 transistors provided adequate gain. Adjusting biasing resistors minimized distortion.
- **Limitations:** The device amplified background noise in louder environments and experienced some distortion at high volumes.
- **Power and Cost:** The design was power-efficient and cost-effective, making it a practical, low-cost alternative to commercial hearing aids.

3. Conclusion

The hearing aid provided clear amplification in quiet environments, with low power consumption and simple assembly. Improvements in noise reduction and distortion control could enhance future versions.

CHAPTER 7

CONCLUSION, APPLICATIONS AND FUTURE ENHANCEMENT

Conclusion

The simple low-cost hearing aid successfully achieved its goal of amplifying weak sounds, providing users with an affordable hearing solution. The circuit, powered by a 3V battery, used readily available components like BC548, BC107, and SK100 transistors to amplify audio signals from a microphone and deliver them through

earphones. The device worked well in quiet environments and offered smooth volume control through a potentiometer. However, challenges like background noise amplification and minor distortion at higher volumes were observed. Overall, the design is cost-effective, energy-efficient, and easy to implement, making it a viable option for individuals in need of basic hearing assistance.

Applications

- **Hearing Assistance:** Ideal for individuals with mild hearing loss who need sound amplification in quiet environments.
- **Low-Cost Solution:** Can be used in developing regions or for low-income individuals where commercial hearing aids are unaffordable.
- **Educational Projects:** The simple design is suitable for students and hobbyists learning about audio amplification and electronics.
- **Portable Audio Amplifier:** The circuit could be adapted as a portable audio amplifier for various applications like enhancing audio from devices.

Future Enhancements

- **Noise Reduction:** Implementing a noise-filtering stage or using a directional microphone could improve performance in noisy environments by reducing background sound amplification.
- **Improved Amplification:** Replacing transistor stages with operational amplifiers (op-amps) could enhance sound quality, reduce distortion at higher volumes, and provide better linearity.
- **Rechargeable Battery:** Switching to a rechargeable lithium-ion battery could extend the operating time and make the device more convenient for long-term use.
- **Compact Design:** Redesigning the circuit with surface-mounted components (SMD) could reduce the size, making the hearing aid more portable and

comfortable for everyday use.

- **Adjustable Frequency Response:** Adding controls to adjust the frequency response could help users tailor the amplification to their specific hearing loss.

REFERENRCES

Books

1. **"Electronic Devices and Circuit Theory"**
Robert L. Boylestad, Louis Nashelsky.
Pearson Education, 2016.
(Covers electronic components and circuit design principles.)
2. **"The Art of Electronics"**
Paul Horowitz, Winfield Hill.
Cambridge University Press, 2015.
(Comprehensive guide on electronic circuit design.)

Journals and Articles

3. **"A Low-Cost Hearing Aid Design Based on Smartphone Technology"**
Hossam A. Mohamed et al.
Journal of Communication and Computer, 2015.
(Discusses low-cost alternatives for hearing aids.)
4. **"Design of a Low-Cost Hearing Aid"**
F. Akhtar et al.
International Journal of Computer Applications, 2016.
(Explores design and implementation of affordable hearing aids.)

Websites

5. **Hearing Loss Association of America (HLAA)**
www.hearingloss.org
(Resources on hearing loss and assistive devices.)
6. **Circuit Basics: How to Build a Simple Hearing Aid**
Circuit Basics
(Guide on components and assembly of a simple hearing aid circuit.)

Standards

7. **ANSI S3.22-2014**
American National Standards Institute.
(Standard specification for hearing aids.)
8. **ISO 8253-1:2010**
International Organization for Standardization.
(Standard for measuring hearing aids performance.)

